


lecture 4

Combinational logic 2


- ROM
- arithmetic circuits
- arithmetic logic unit (ALU)

Last lecture: truth tables, logic gates & circuits


AND

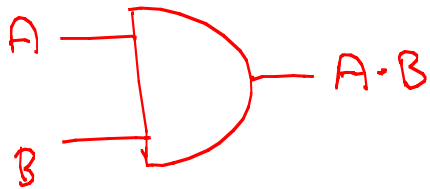


OR

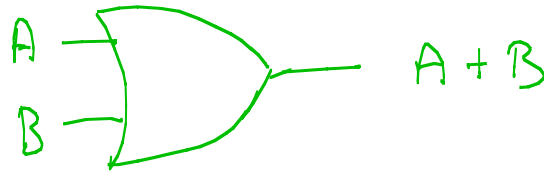


NOT

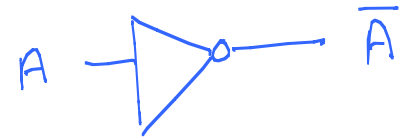


NAND

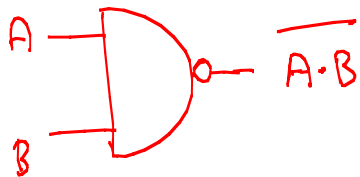

NOR

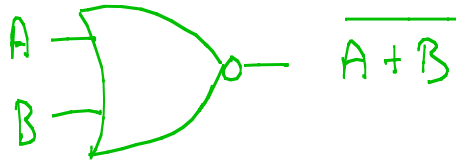


XOR

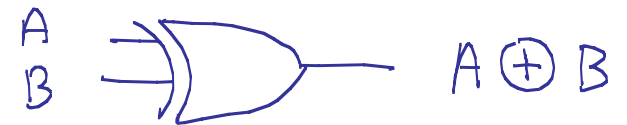

Recall multiplexor (selector)

$$Y = \overline{S} \cdot A + S \cdot B$$

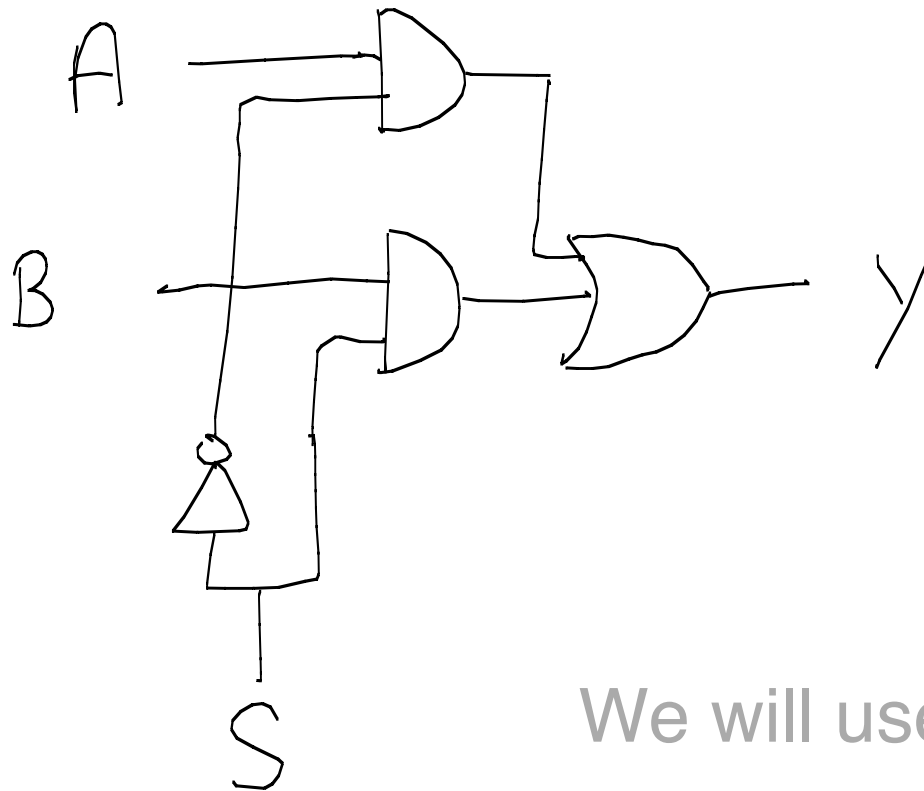

if S
Y = B
else
Y = A

We will use this several times later.

"Read-only Memory"

(leftover topic from last lecture)


A_1	A_0	Y_2	Y_1	Y_0
0	0	0	1	1
0	1	0	0	1
1	0	0	0	0
1	1	1	0	0

address

data

Sometimes we can think of a circuit as a "hardwired" memory (read only).

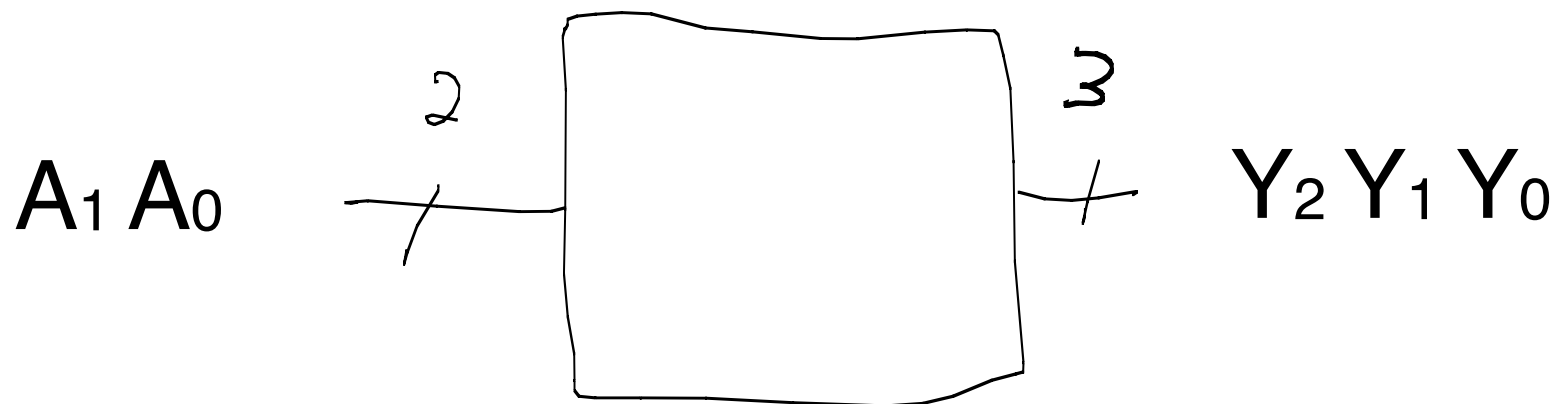Note: the order of the A_1 A_0 variables matters.



Recall: binary arithmetic

$$\begin{array}{r} C_{n-1} \dots C_2 C_1 C_0 \\ A_{n-1} \dots A_2 A_1 A_0 \\ + B_{n-1} \dots B_2 B_1 B_0 \\ \hline S_{n-1} \dots S_2 S_1 S_0 \end{array}$$

Notes:

- $C_0 = 0$
- A, B could represent signed or unsigned numbers

Let's build an "adder" circuit.

$$\begin{array}{r}
 C_{n-1} \dots C_2 C_1 \\
 A_{n-1} \dots A_2 A_1 A_0 \\
 B_{n-1} \dots B_2 B_1 B_0 \\
 \hline
 S_{n-1} \dots S_2 S_1 S_0
 \end{array}$$

$A_0 B_0$		$S_0 C_1$	
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


$$S_0 =$$

$$C_1 =$$

Half Adder

$$S = A \oplus B$$

$$C = A \cdot B$$

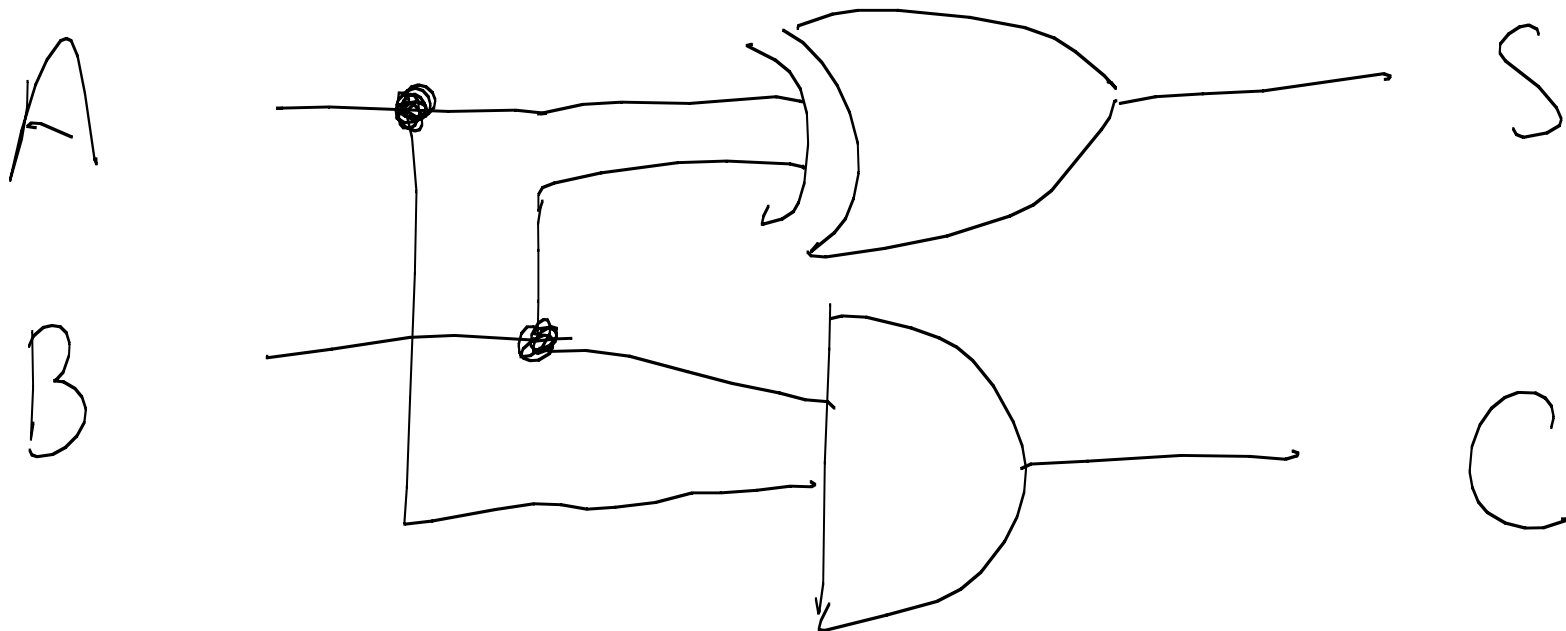


$C_{n-1} \dots C_2 C_1 C_0$

$A_{n-1} \dots A_2 A_1 A_0$

$B_{n-1} \dots B_2 B_1 B_0$


$S_{n-1} \dots S_2 S_1 S_0$

full adder

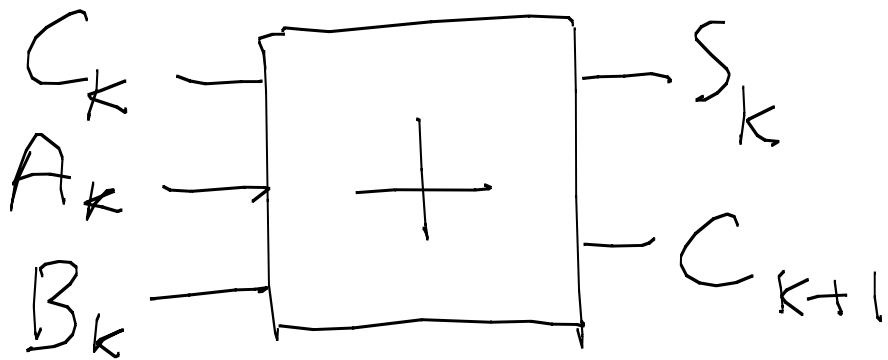

A_k	B_k	C_k	S_k	C_{k+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Ripple Adder

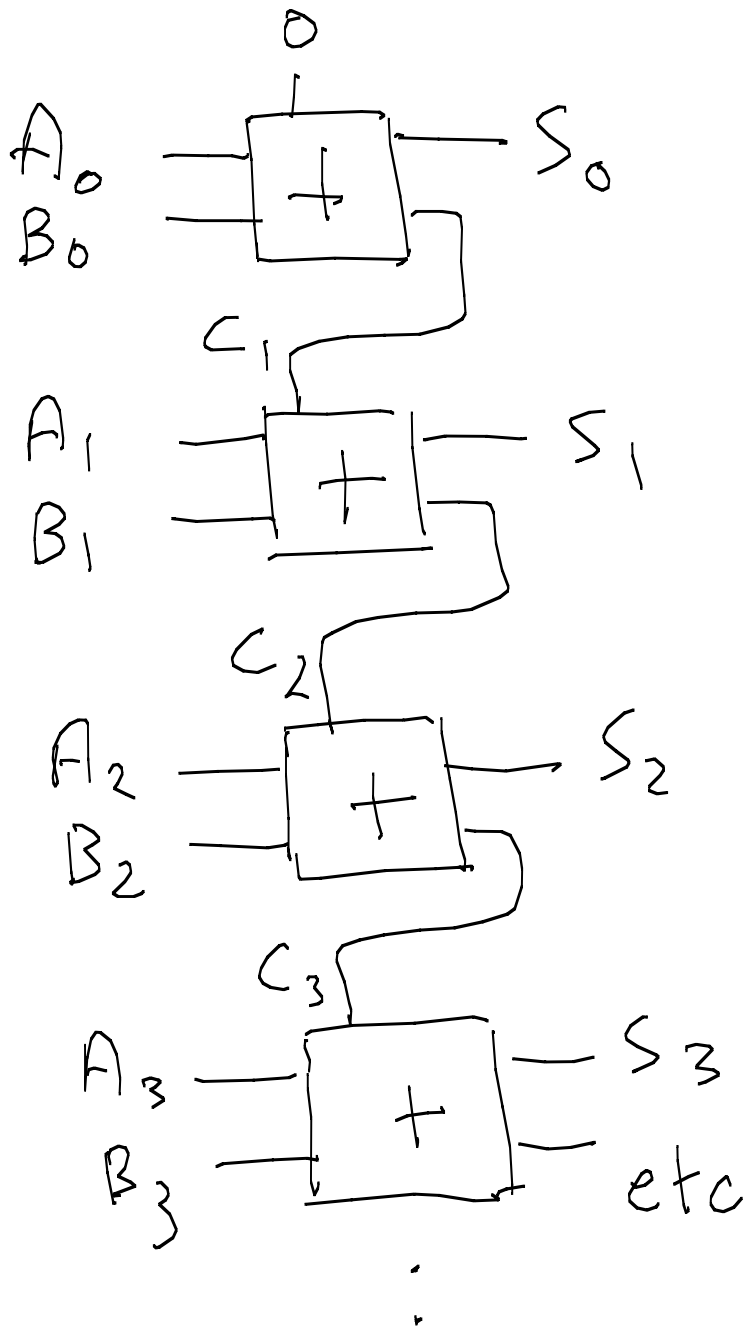

If $n = 32$, then we can have a long delay as carries propagate through the circuit. We'll return to this later.

$$\begin{array}{r}
 C_{n-1} \dots C_2 C_1 C_0 \\
 A_{n-1} \dots A_2 A_1 A_0 \\
 + B_{n-1} \dots B_2 B_1 B_0 \\
 \hline
 S_{n-1} \dots S_2 S_1 S_0
 \end{array}$$

As I mentioned before.... the *interpretation* of the S bit string depends on whether the A and B bit strings are signed or unsigned.


However, the full adder circuit does not depend on whether A and B are signed or unsigned.

Overflow

We still might want to know if we have "overflowed" :

- e.g. - if the sum of two positive numbers yields a negative
- if the sum of two negative numbers yields a positive

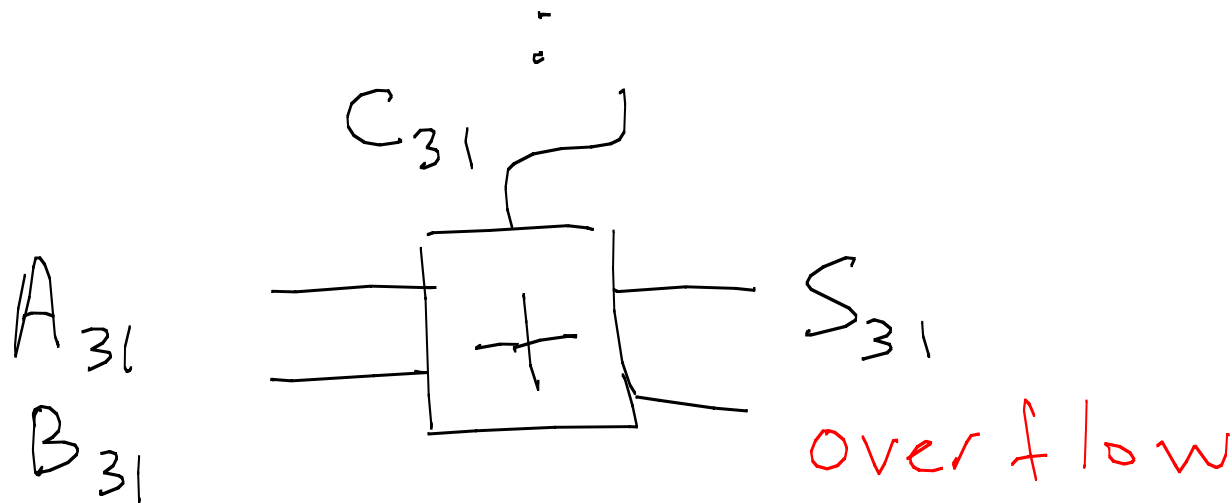
How can we detect these two cases ? (see Exercises 2)



TODO TODAY

- encoder
- decoder
- n-bit multiplexor
- fast adder
- ALU

Encoder

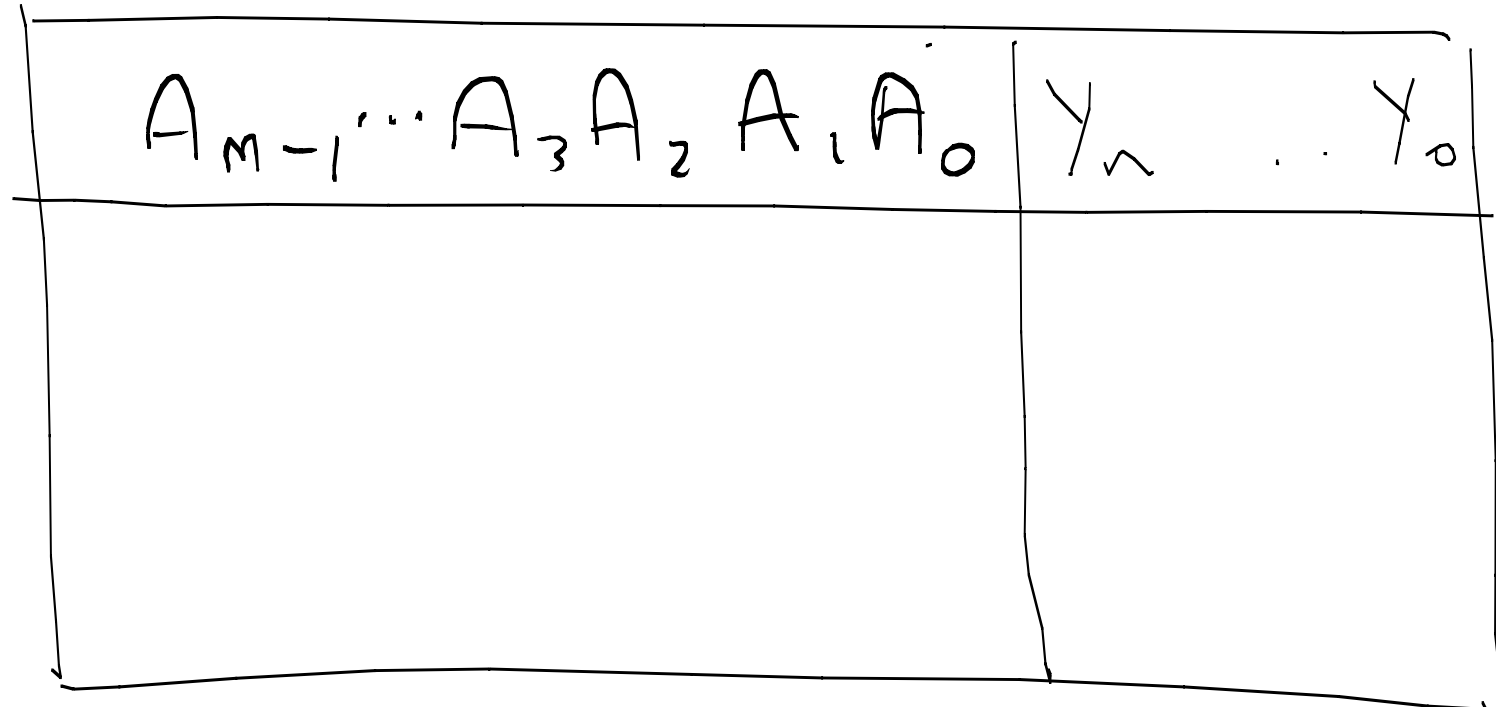


many bits

code
(few bits)

Encoder Example 1


panel with
five buttons

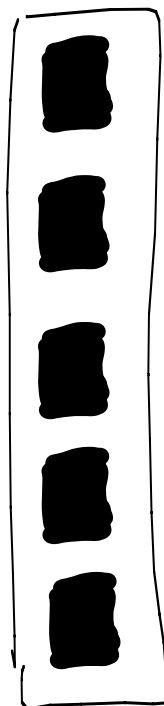

b_4	b_3	b_2	b_1	b_0	y_2	y_1	y_0
0	0	0	0	1	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	1	0	0	0	0	1	1
1	0	0	0	0	1	0	0

This assumes only one button can be pressed at any time.

panel with
five buttons

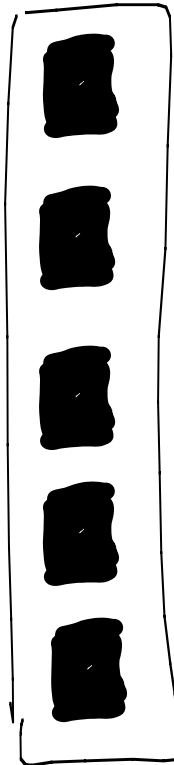


b_4	b_3	b_2	b_1	b_0	y_2	y_1	y_0
0	0	0	0	0	0	0	0
X	X	X	X	1	0	0	1
X	X	X	1	0	0	1	0
X	X	1	0	0	0	1	1
X	1	0	0	0	1	0	0
1	0	0	0	0	1	0	1


This allows two buttons to be pressed at the same time (and encodes the one with the highest index).

Encoder Example 2


panel with
ten buttons

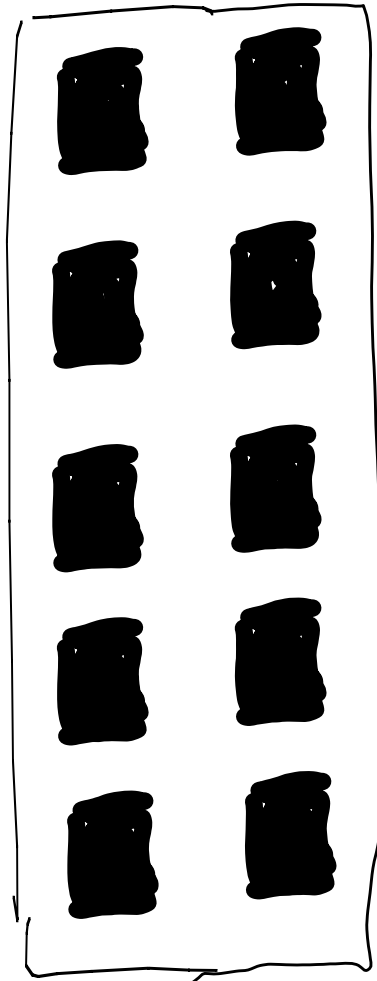

6 9 0 0 0 0

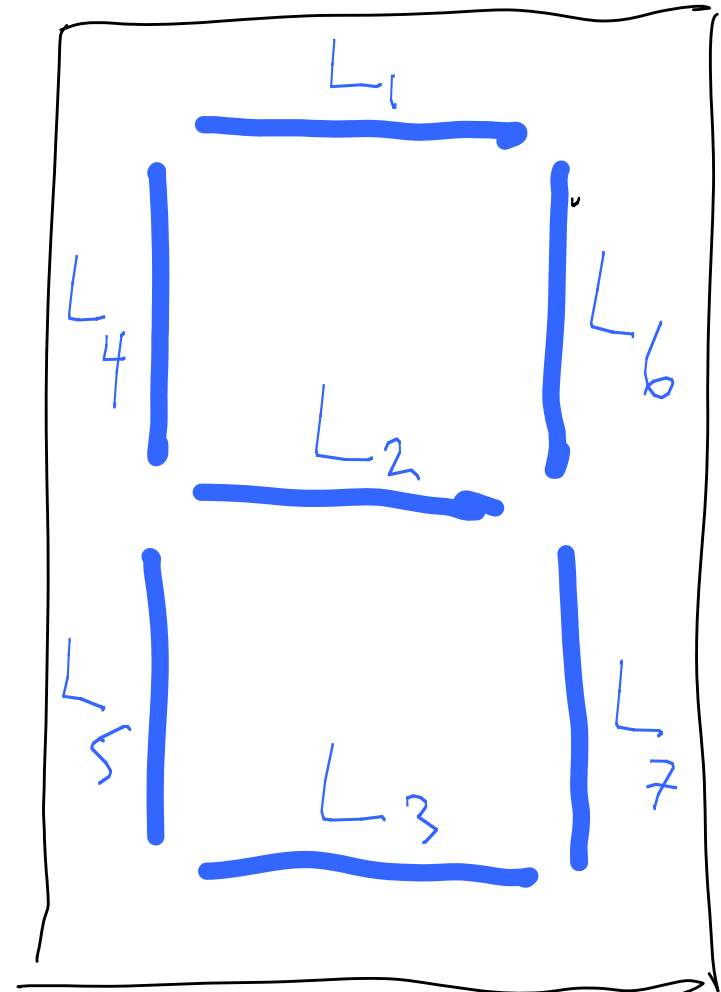

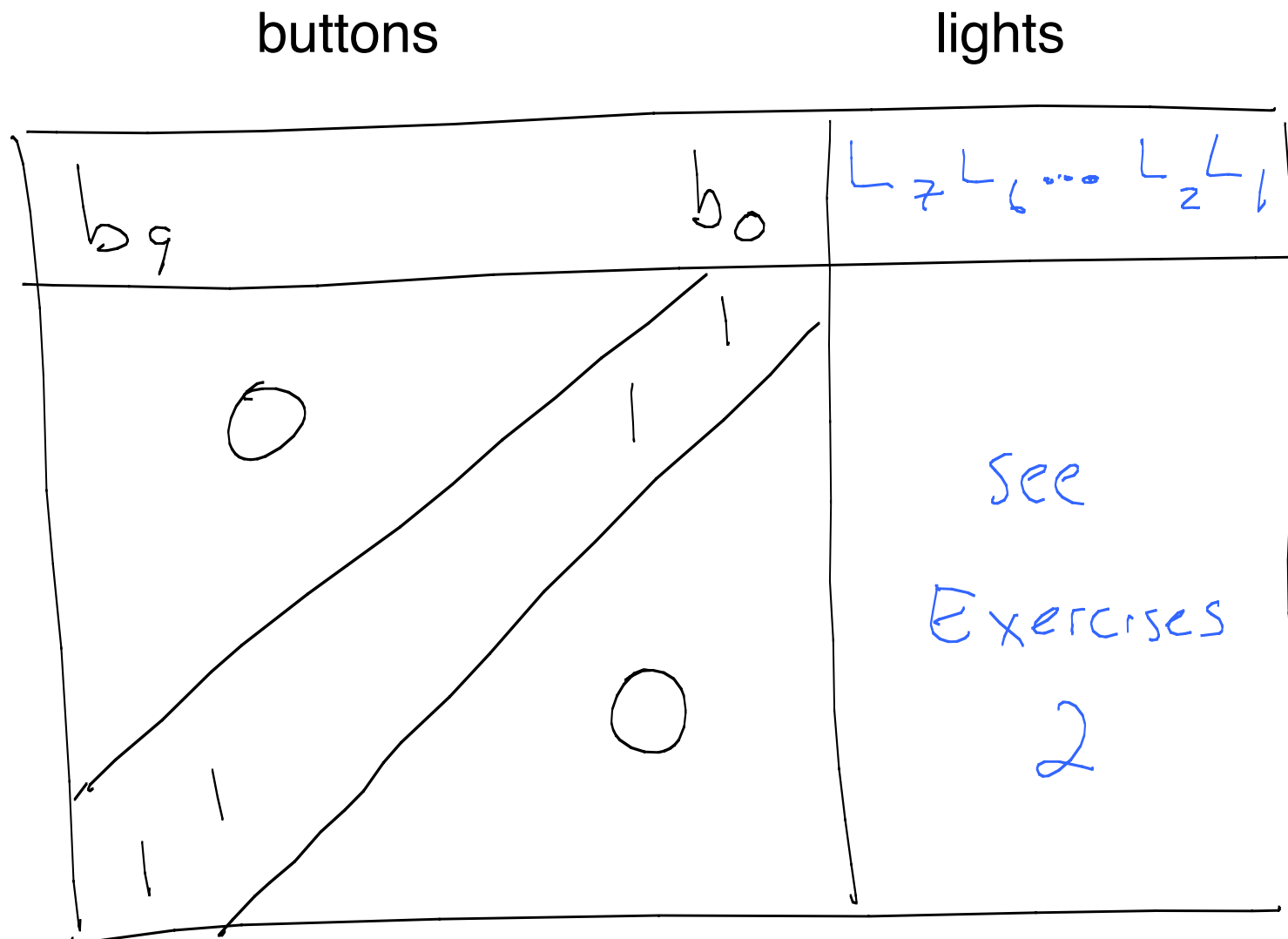display e.g. on a
digital watch,
calculator, etc.





Each light L_i is turned on (1) by some set of button presses.

Each button b_k turns on (1) some set of lights.


Decoder

b_2 b_1 b_0	y_7	...	y_2	y_1	y_0
0 0 0	1				
0 0 1		1			
0 1 0			1		
0 1 1				1	
1 0 0					1
1 0 1				1	
1 1 0					1
1 1 1					1

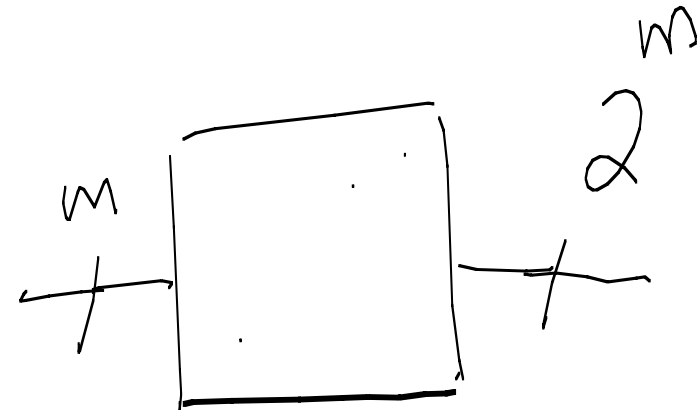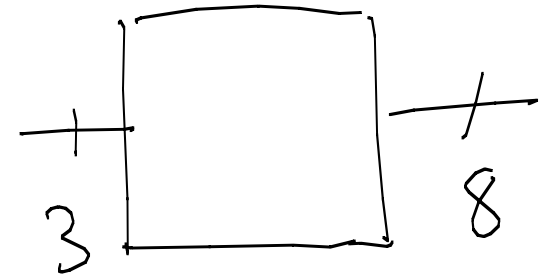
code word (in this example, it specifies which output is 1)




2-bit multiplexor

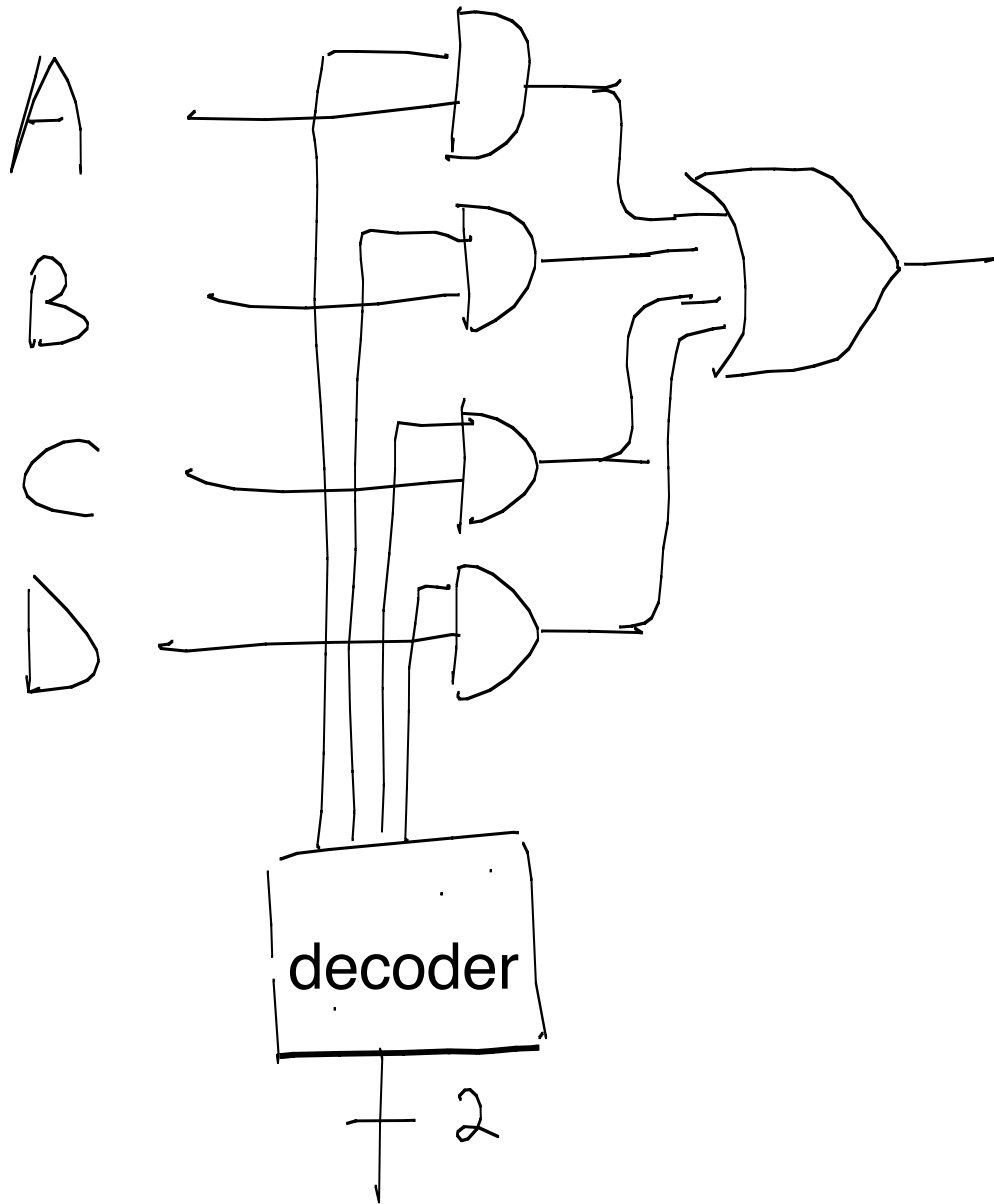

Notation:

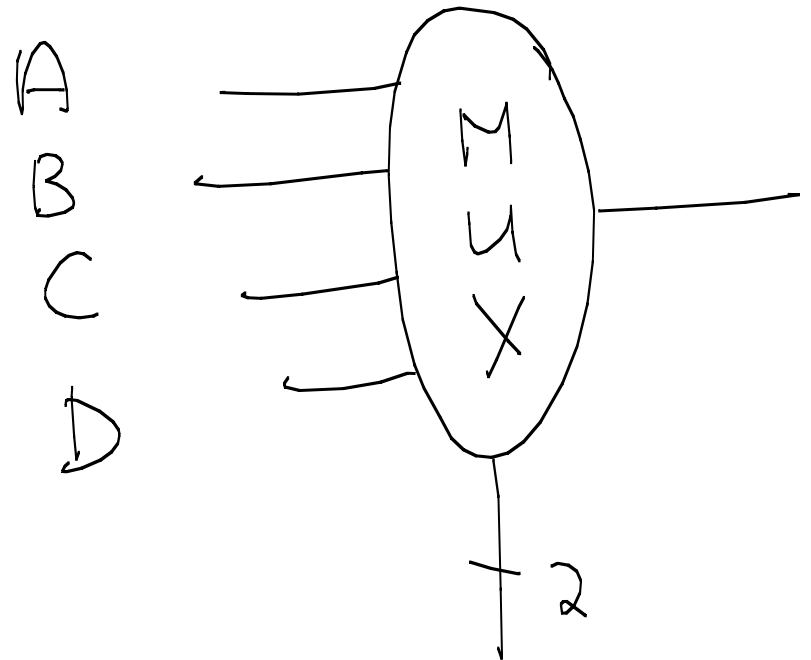


More general example (2-bit multiplexor)

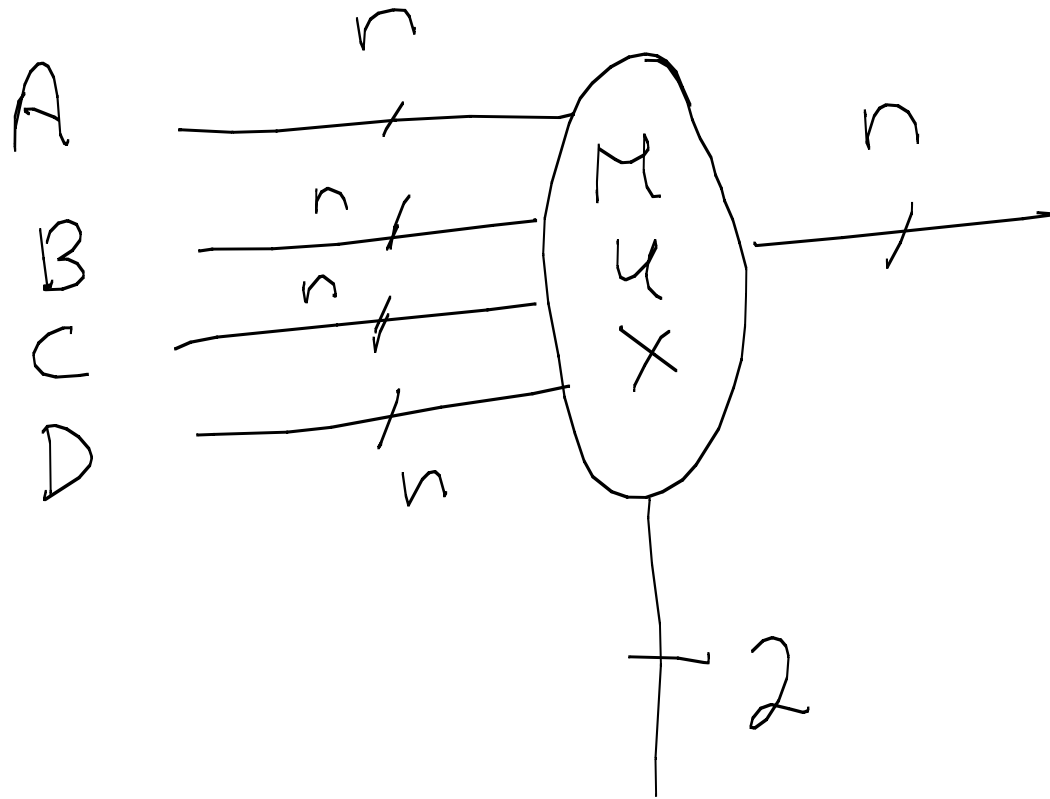

Selects from four n -bit inputs. For each A_i , B_i , C_i , D_i , we replicate the circuit on the previous slide, but use the same decoder circuit.

n-bit multiplexor


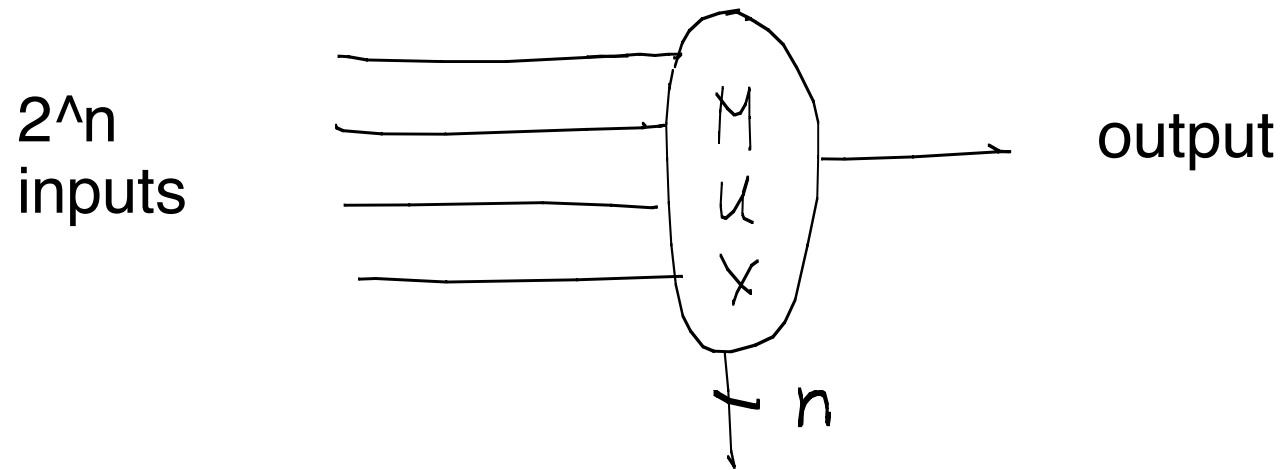


which
input?


We will next look at some examples of how multiplexors are used.

Recall the ripple adder.

The main problem is that it is slow.

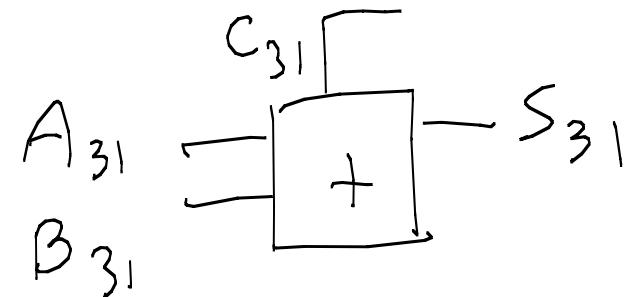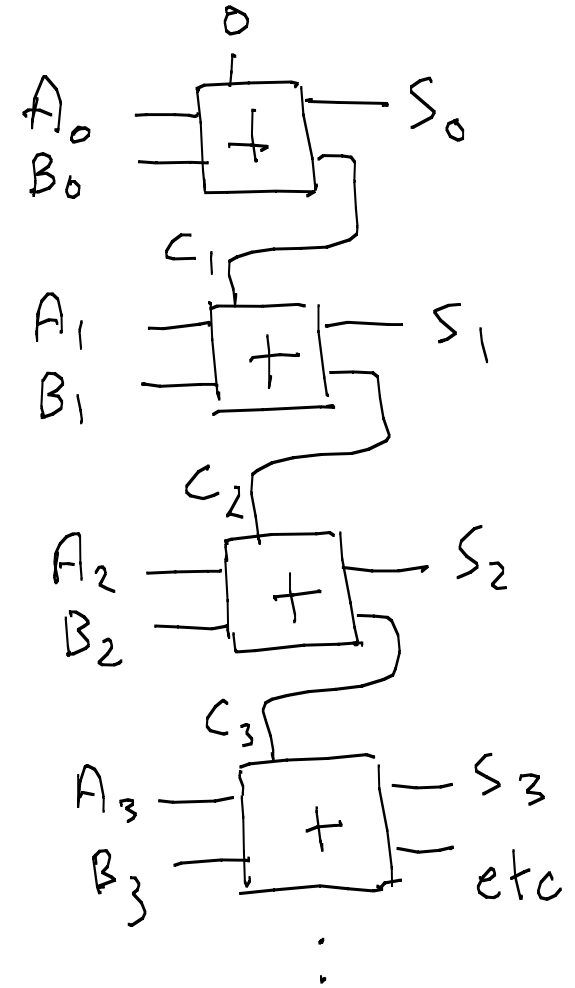


How to speed up the adder ?

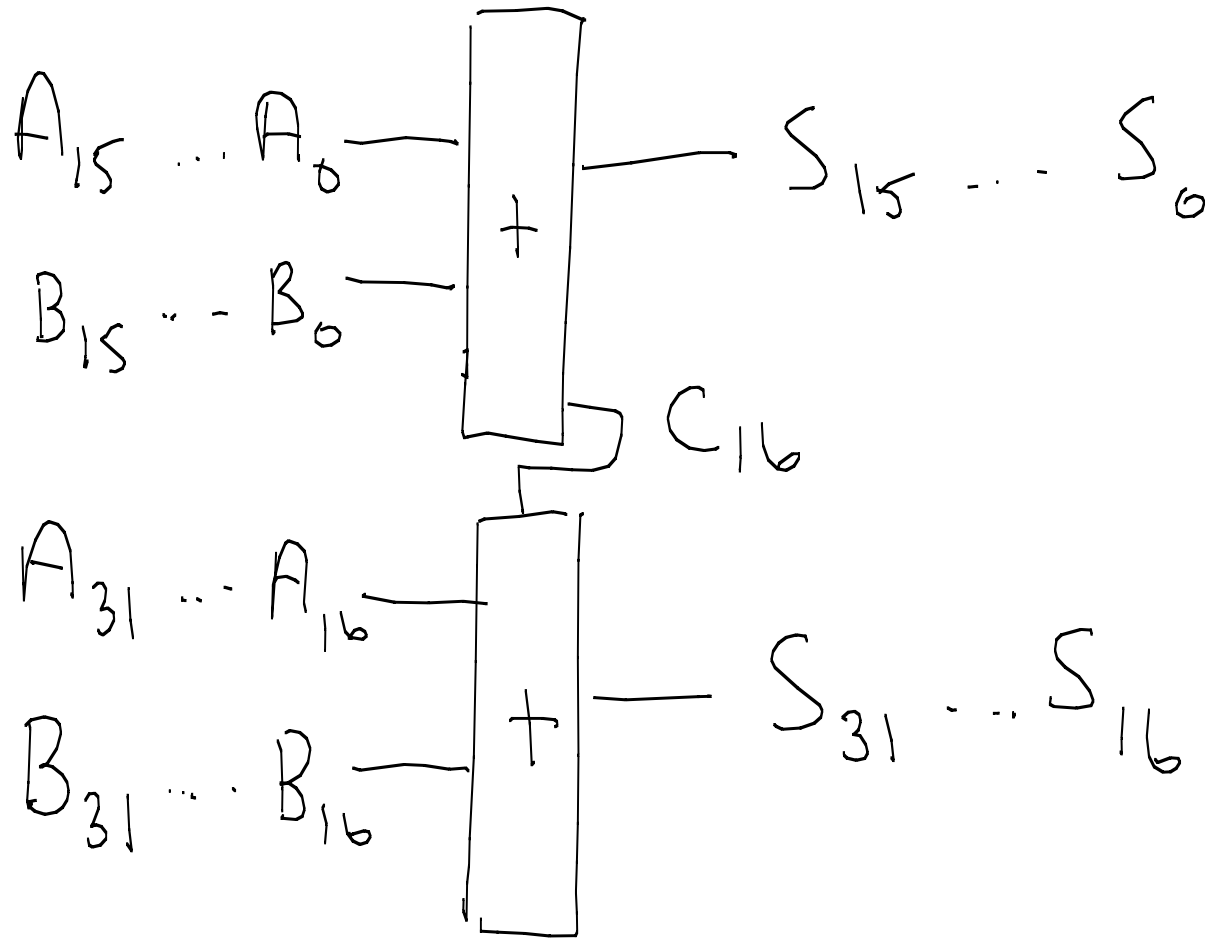

Instead of one 32 bit adder, think of two 16 bit adders.

We can compute the result of each, in half the time. (However, if $C_{16} = 1$, then we have to wait for it to ripple through.)

Fast Adder

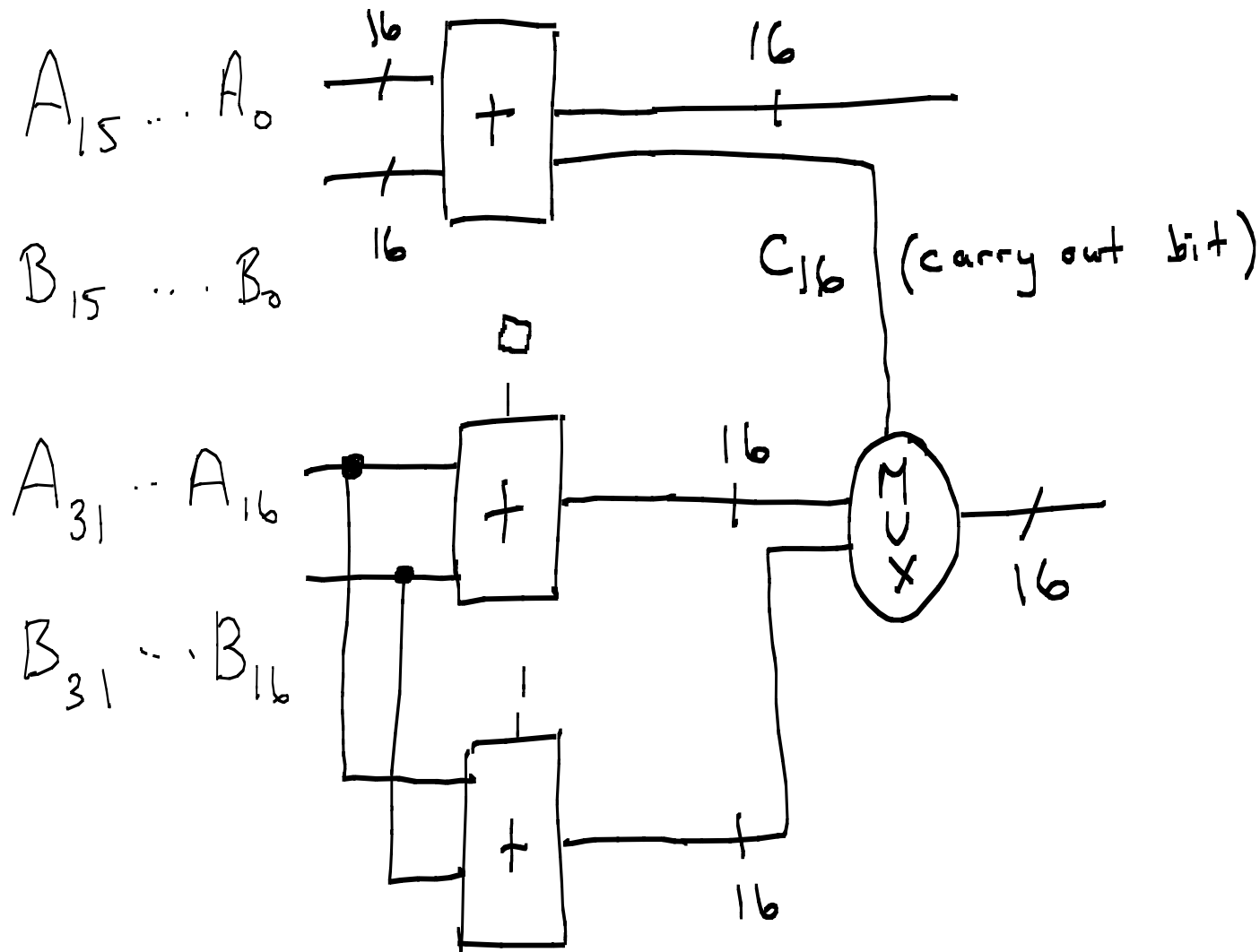

Tradeoffs: we chop the time in half (almost, why?) but it increases the number of gates by more than 50% (why?). Note we can repeat this idea (recursion).



Subtraction

$$\begin{array}{r} A_{n-1} \dots A_2 A_1 A_0 \\ - B_{n-1} \dots B_2 B_1 B_0 \\ \hline S_{n-1} \dots S_2 S_1 S_0 \end{array}$$

$$x - y = x + (-y)$$


↑

Invert bits and add 1.

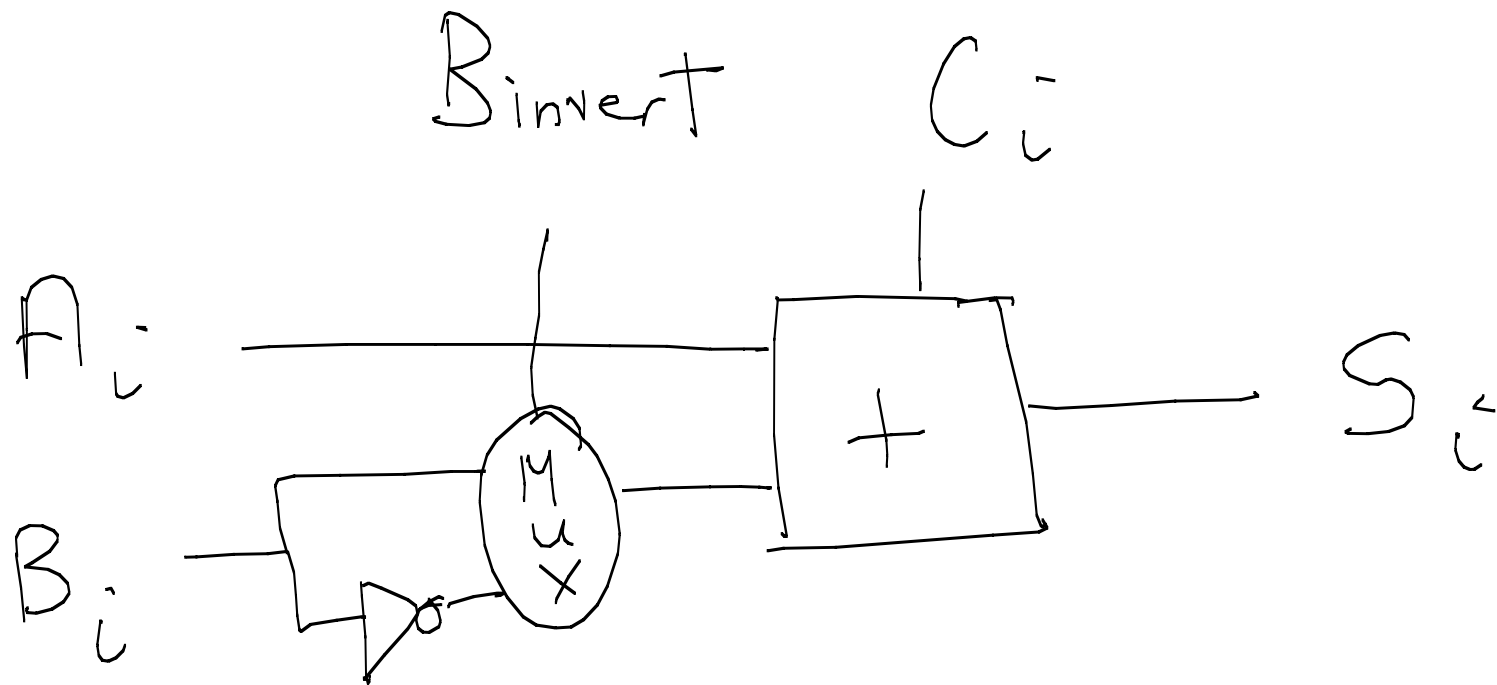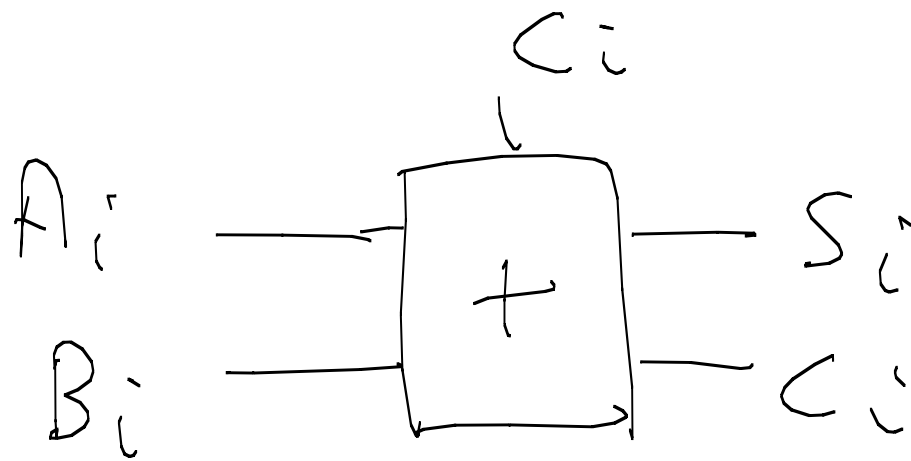


Invert bits and add 1.

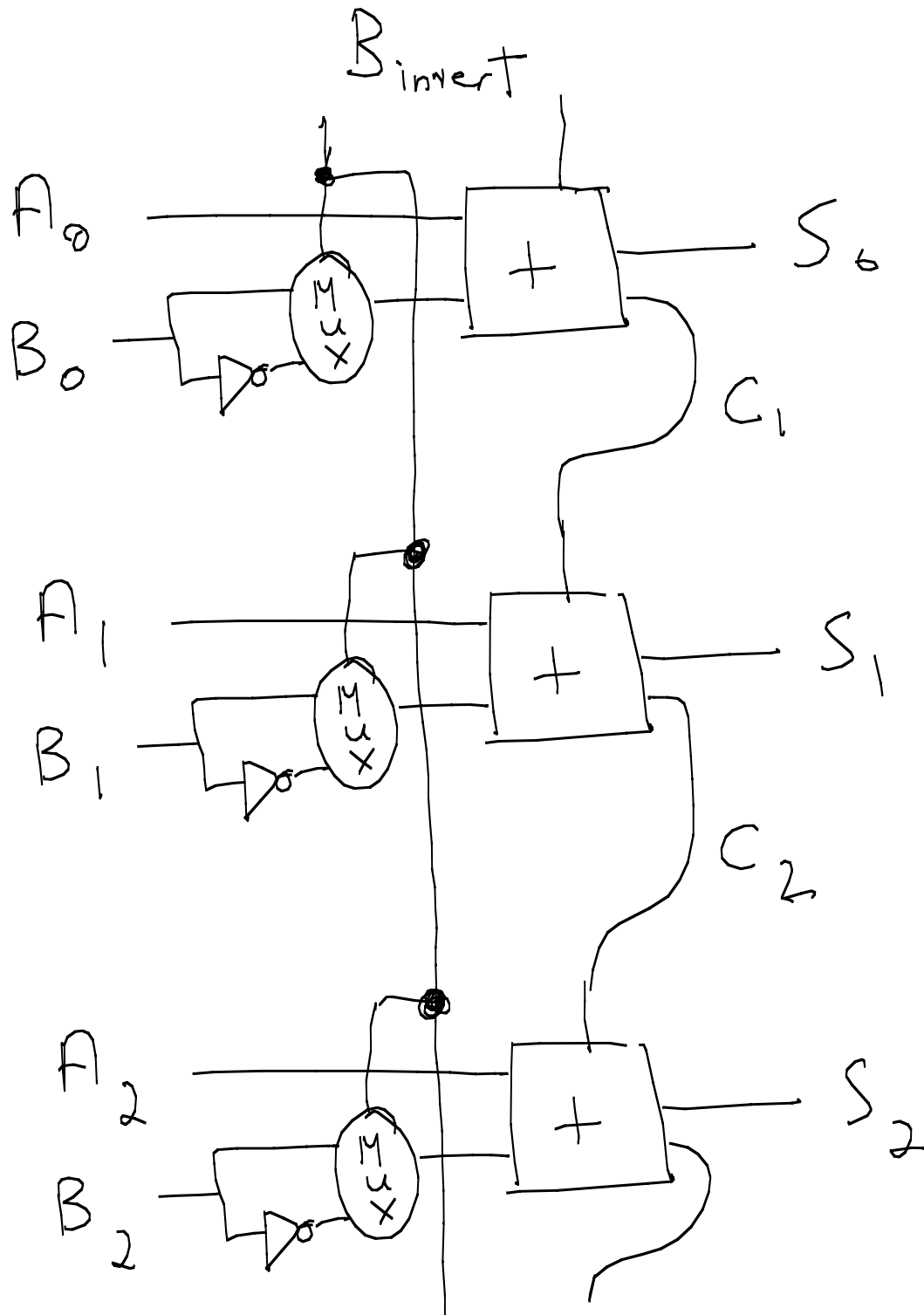When B_{invert} is 1, this adds 1 by setting C_0 to 1.



$$\begin{array}{r}
 A_{n-1} \dots A_2 A_1 A_0 \\
 B_{n-1} \dots B_2 B_1 B_0 \\
 \hline
 S_{n-1} \dots S_2 S_1 S_0
 \end{array}$$


$n = 32$

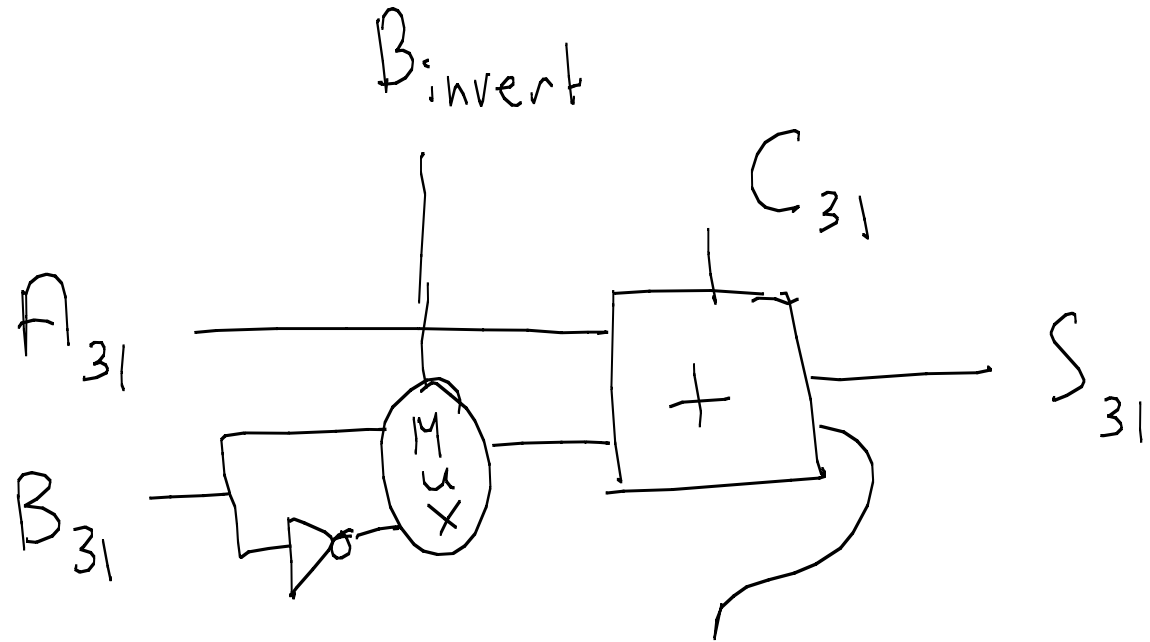

B_{invert}	A_{31}	B_{31}	S_{31}	overflow
0				
1				

See Exercises 2

Let's include a bitwise AND and OR.

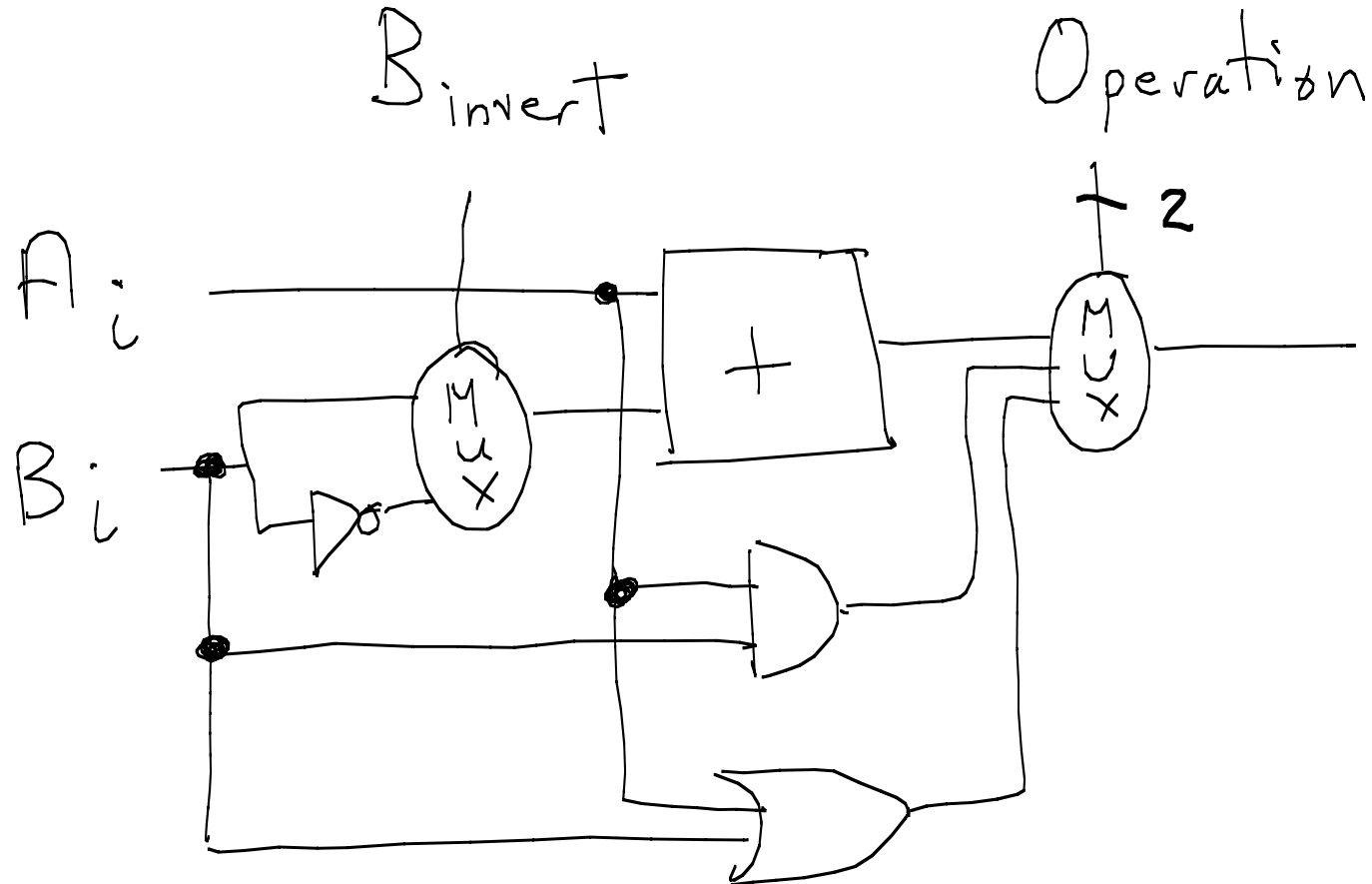

Arithmetic Logic Unit (ALU)

